

CECS 341

Fair Nuri Aboshehwa

LAB 4C

## Section 1: Module Source Code

```
module ALUwithControl (ALUOp, FuncCode, A, B, ALUOut, Zero);
  input      [1:0]  ALUOp;
  input [5:0]  FuncCode;
  input      [31:0] A;
  input      [31:0] B;
  output     [31:0] ALUOut;
  output     [31:0] Zero;
  wire       [3:0]  ALUctl;

  ALUControl Lab2b (ALUOp, FuncCode, ALUctl);
  ALU      Lab2a (ALUctl, A, B, ALUOut, Zero);
Endmodule
```

## Section 2: Test Fixture

```
`timescale 1ns / 1ps
```

```
module ALUwithControlTester;
```

```
    reg [1:0]    ALUOp;  
    reg [5:0]    FuncCode;  
    reg [31:0]   A;  
    reg [31:0]   B;  
    wire [31:0]  ALUOut;  
    wire [31:0]  Zero;
```

```
        ALUwithControl uut (  
        .ALUOp(ALUOp),  
        .FuncCode(FuncCode),  
        .A(A),  
        .B(B),  
        .ALUOut(ALUOut),  
        .Zero(Zero)  
        );
```

```
initial begin  
    $dumpfile("dump.vcd");  
    $dumpvars(5);  
end
```

```
        initial begin  
            ALUOp = 2'b00;  
            A = 32'h55555555;  
            B = 32'haaaaaaaaab;  
            FuncCode = 6'b000000;  
            #10;
```

```
        ALUOp = 2'b00;  
        A = 32'h55555555;  
        B = 32'haaaaaaaaab;  
        FuncCode = 6'b100000;  
        #10;
```

```
        ALUOp = 2'b10;  
        A = 32'h55555555;  
        B = 32'haaaaaaaaab;
```

```

    FuncCode = 6'b100010;
        #10;

    ALUOp = 2'b10;
    A = 32'h55555555;
    B = 32'haaaaaaaa;
    FuncCode = 6'b100101;
        #10;

    ALUOp = 2'b10;
    A = 32'h55555555;
    B = 32'haaaaaaaa;
    FuncCode = 6'b101010;
        #10;

    $stop;

end
endmodule

```

### Section 3: Wave Form Screenshot

